

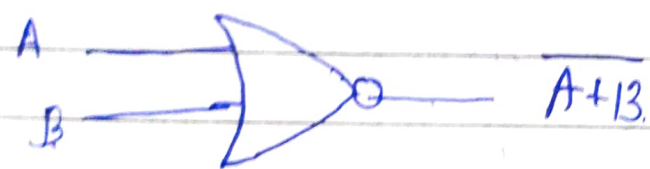



09 Mar 2022

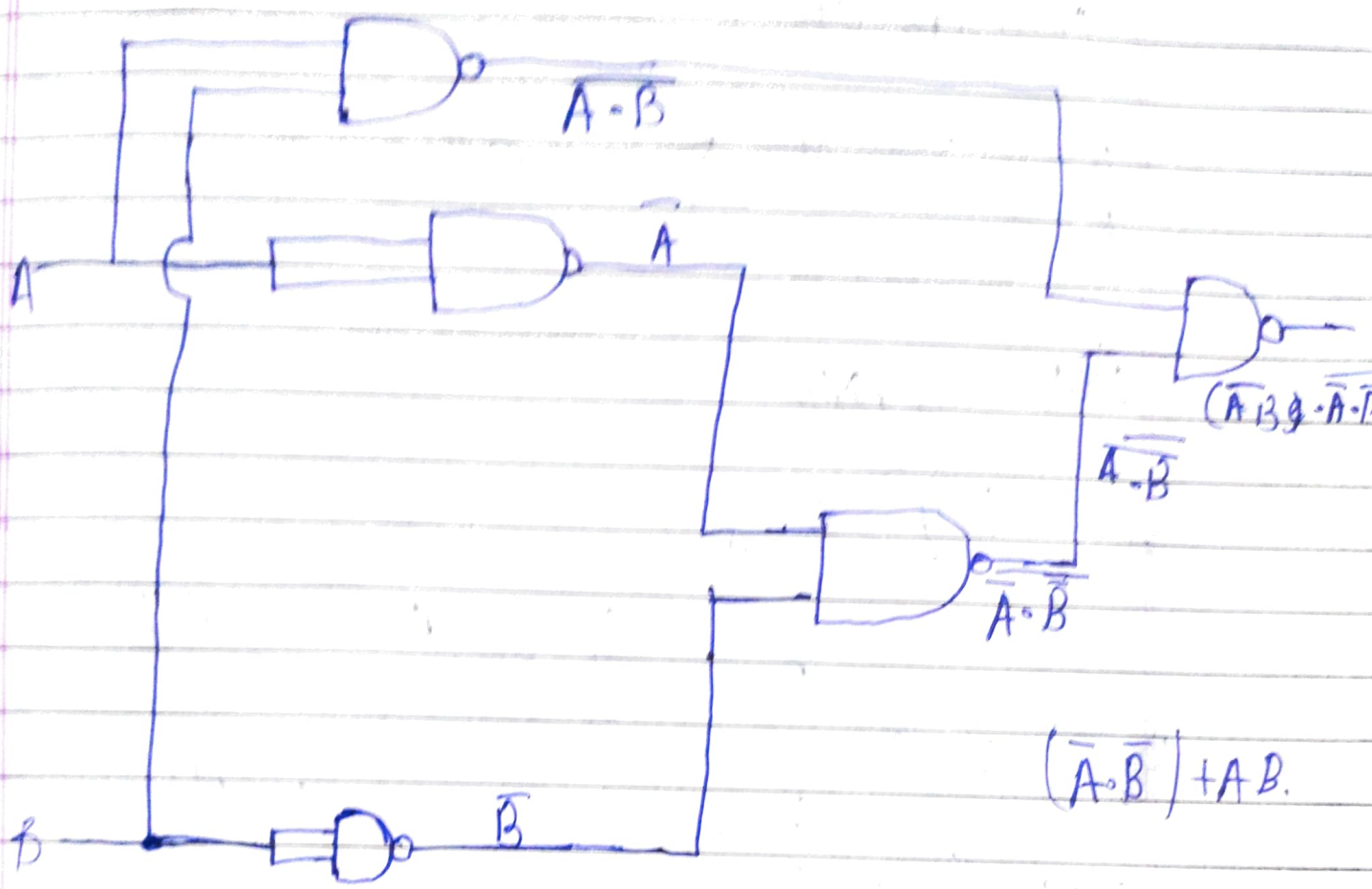


⑥ NOR as NOT

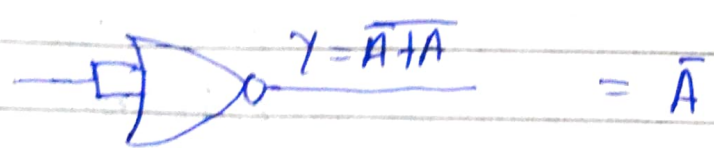


⑦ NOR as OR

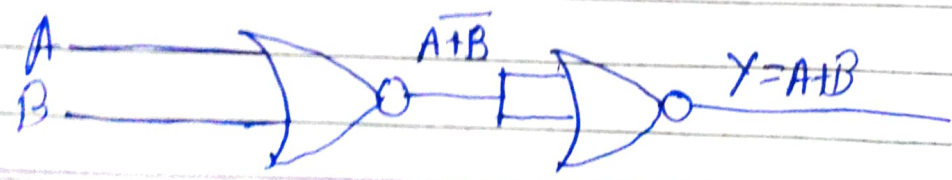


NOR as OR

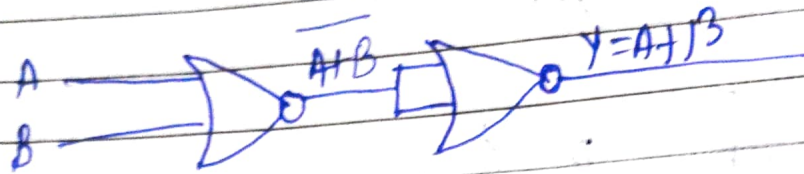

NOR as AND

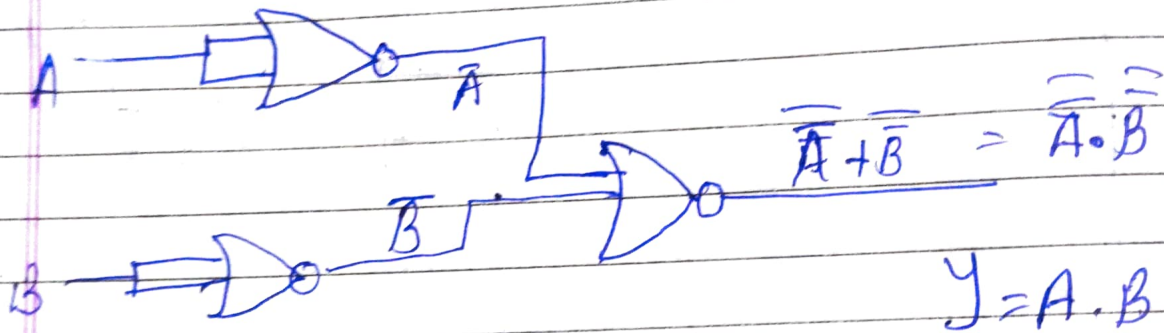

NOR as NAND

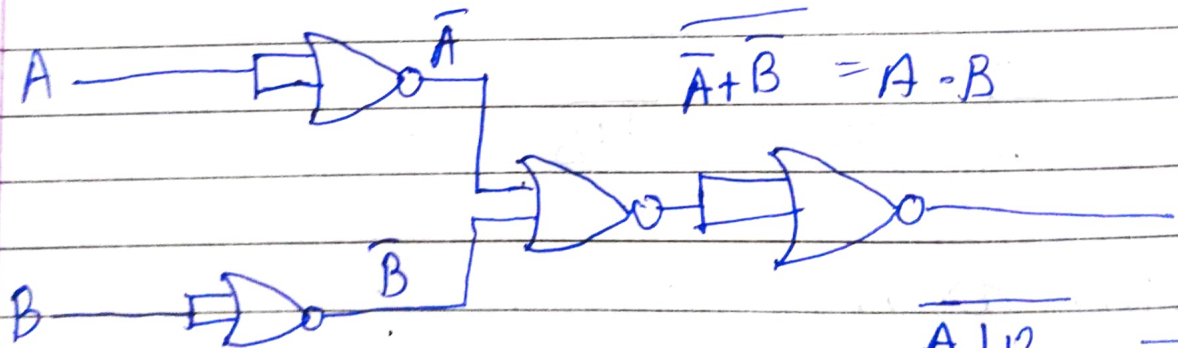


$$\begin{aligned} &\overline{A+B} \rightarrow \text{NOR} \\ &A\bar{B} + \bar{A}B \\ &A\bar{B} + \bar{A}B \end{aligned}$$

NOR as EXOR

\* NOR as EX-OR

$\overline{A+B}$  NOR
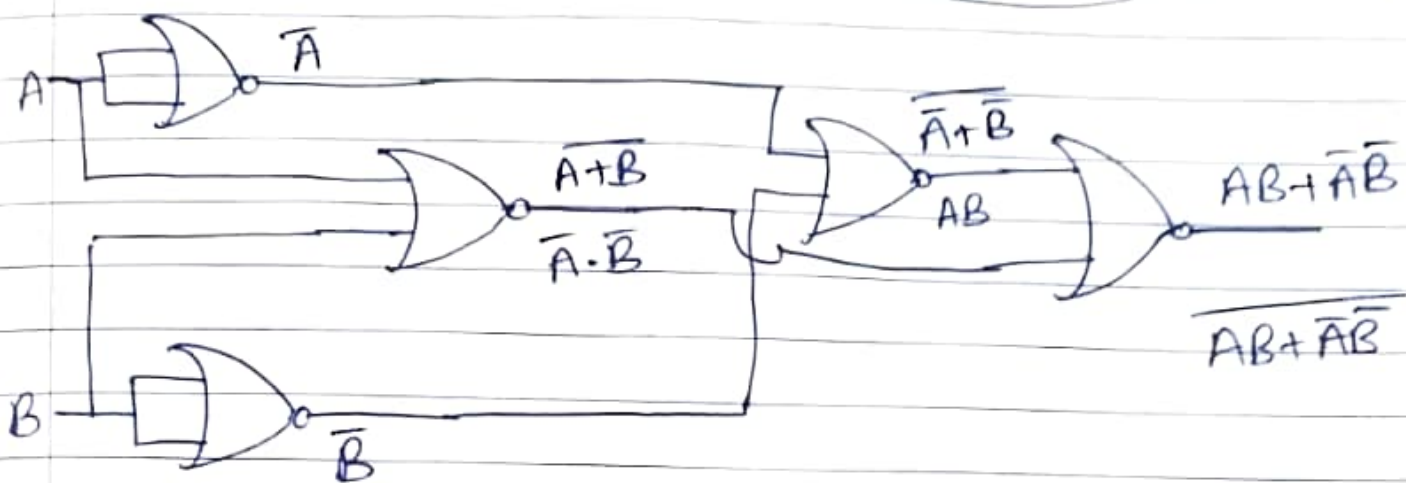
$$\overline{AB + \overline{A}\overline{B}}$$



\*  $A + B \cdot C \rightarrow$   
 $= (A+B) \cdot (A+C)$

$$\underline{A \cdot A} + A \cdot C + B \cdot A + B \cdot C$$


$$\underline{A + AC + BA + BC}$$

$$A(1 + \underline{C} + B) + BC$$

$$A(1) + BC$$

$$A + B \cdot C$$

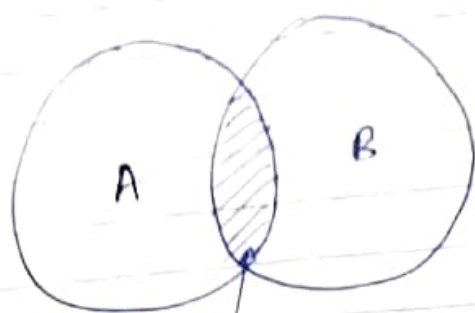\*  $A + AB = A(1 + B)$   
 $= A(1)$   
 $= A$



$$A + A \cdot B = A + AB = A.$$

$$* \quad A + \bar{A}B = \underline{A + B}$$

$$(A + \bar{A}) \cdot (A + B)$$

$$A + \bar{A} = 1$$

$$(1) \cdot (A + B) = A + B$$

\* Compute

$$\bar{A} + AB + ABC + ABCD$$

~~Recall~~

$$\bar{A} + AB(1 + C + CD) = \bar{A} + AB$$

$$(\bar{A} + A) \cdot (\bar{A} + B)$$

$$1 \cdot (\bar{A} + B)$$

$$= \underline{\bar{A} + B}$$

$$* \text{ If } \bar{A} + AB + ABC + ABCD + 1$$

$$= 1$$

1 or with any expression will be

1

\* Importance of Simplification of Algebraic Equation.

$$Y = \bar{A} + AB + ABC + ABCD$$

$$= \bar{A} + B$$



Q  $Y = AB + C\bar{D} + D + BC + (C + \bar{C}) + \bar{B}A$

$$Y = A(B + \bar{B}) + D + BC + 1 + \bar{B}A$$

$$\boxed{Y = 1}$$

Q  $Y = (\overline{A+B} + \overline{B \cdot C} + \bar{C} + B + B\bar{C} + \bar{D} + \overline{A+C})$

$$Y = \bar{A} \cdot \bar{B} + \bar{B} + \bar{C} + \bar{C} + B + B\bar{C} + \bar{D} + \overline{A+C}$$

$$Y = 1$$

Q  $Y = (A + (BC)')' (AB' + ABC)$

~~$$Y = (A \cdot (BC)') \cdot A$$~~

$$Y = (A' \cdot ((BC)'))' (AB' + BC)$$

$$= (A' \cdot (BC)) \cdot (A(B' + C))$$



$$A' = 0 = (A' \cdot BC) A \cdot (B' + C) = 0$$



$$\begin{aligned}
 Q \quad & xy z + x' y + x y z' \\
 &= xy(z + z') + x' y \\
 &= xy + x' y \\
 &= y(x + x') \\
 &= y(1) = \underline{\underline{y}}
 \end{aligned}$$

Q Design a circuit.

$$F = xy + x'y' + y'z$$

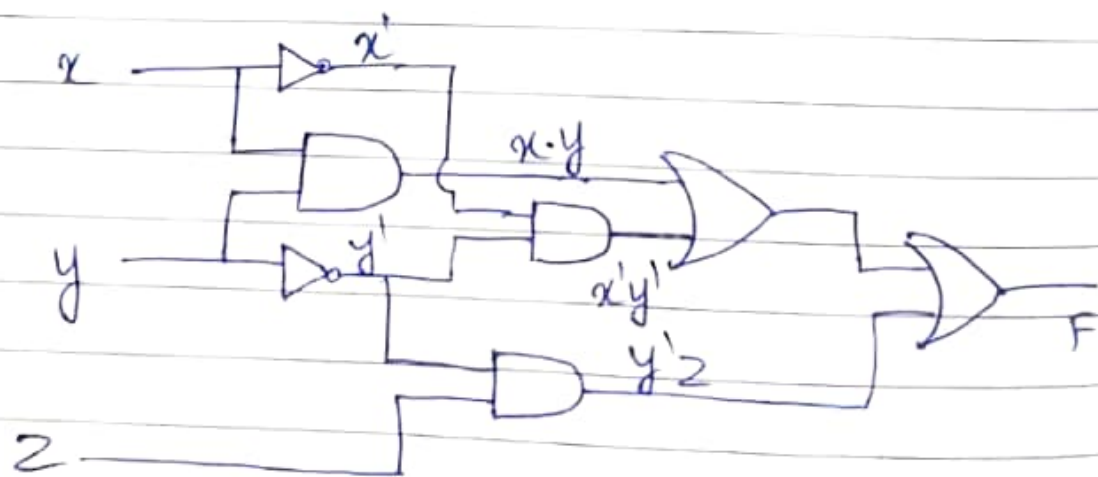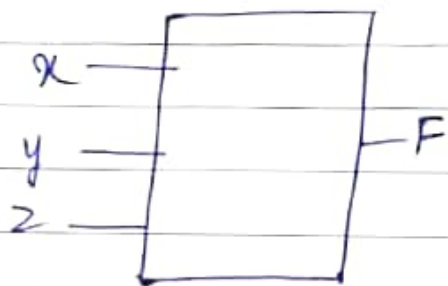

2-input OR  
 2-input AND  
 NOT

Q Design the same ckt using OR and not gate.

$$F = xy + x'y' + y'z$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$


$$F = \overline{\overline{xy + x'y' + y'z}}$$

~~\* \* \* \* \*~~

$$xy = \overline{\overline{x + y}}$$

$$= \overline{\overline{x}} \cdot \overline{\overline{y}} = xy$$
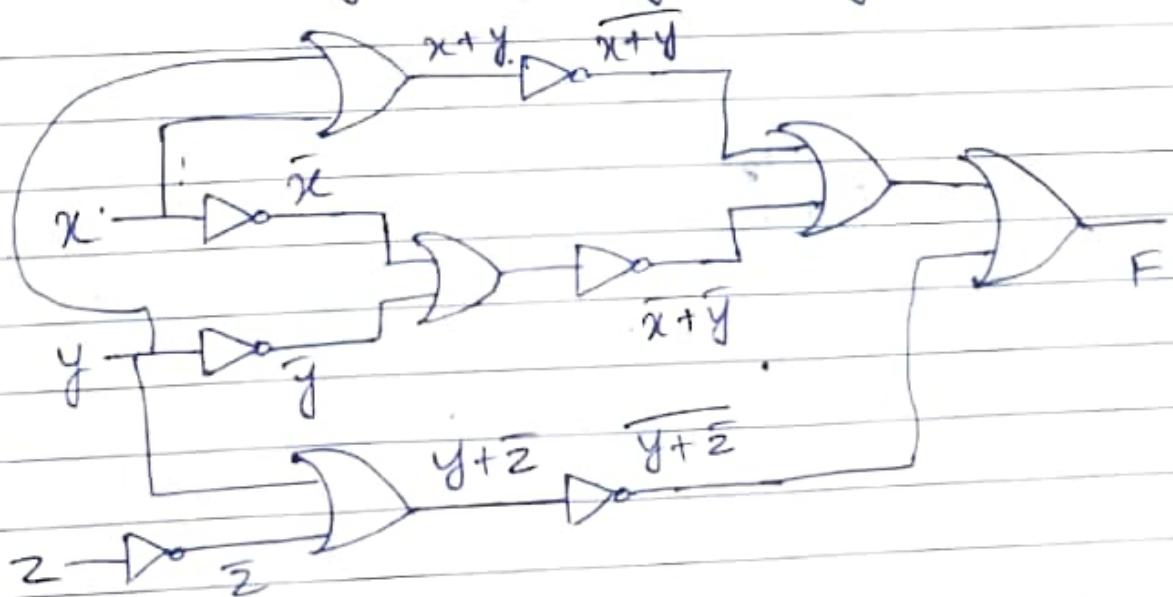
$$F = (\overline{\overline{x + y}}) + (\overline{\overline{x + y}}) + (\overline{\overline{y + z}})$$




$$\begin{aligned}
 F &= \overline{xy + x'y' + y'z} \\
 &= \overline{(\overline{x}y) \cdot (\overline{x'y' + y'z})} \\
 &= \overline{(\overline{x} + y) \cdot (\overline{x} \cdot y \cdot y'z)} \\
 &= \overline{(\overline{x} + y) \cdot ((\overline{x} + \overline{y}) \cdot (y + z))} \\
 &= \overline{(\overline{x} + y)} + \overline{(x + y)} + \overline{(y + z)}
 \end{aligned}$$


$$\overline{A+B+C} = \overline{A} \cdot \overline{B} \cdot \overline{C}$$

$$\overline{A \cdot B \cdot C} = \overline{A} + \overline{B} + \overline{C}$$

CK + Problem

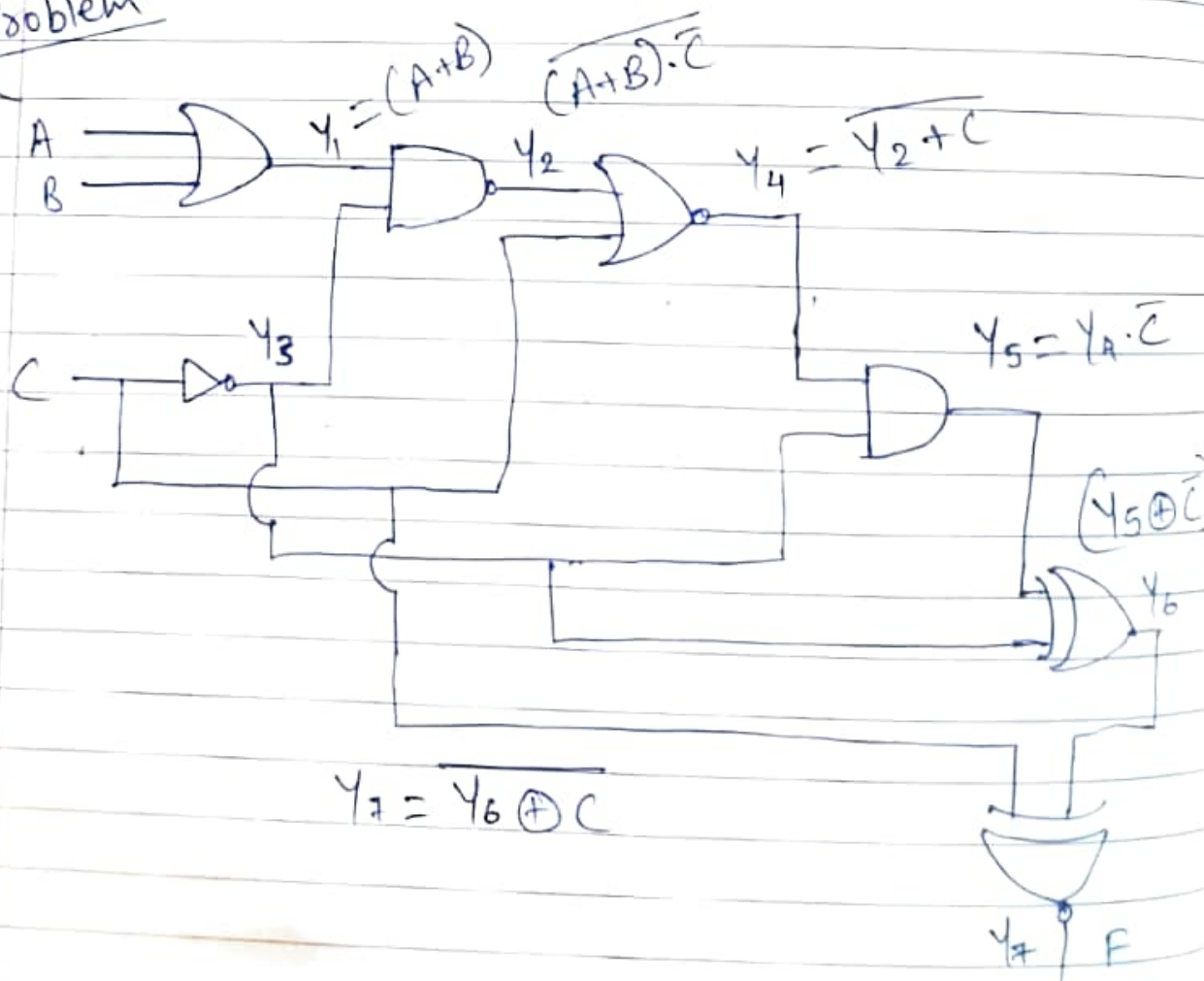



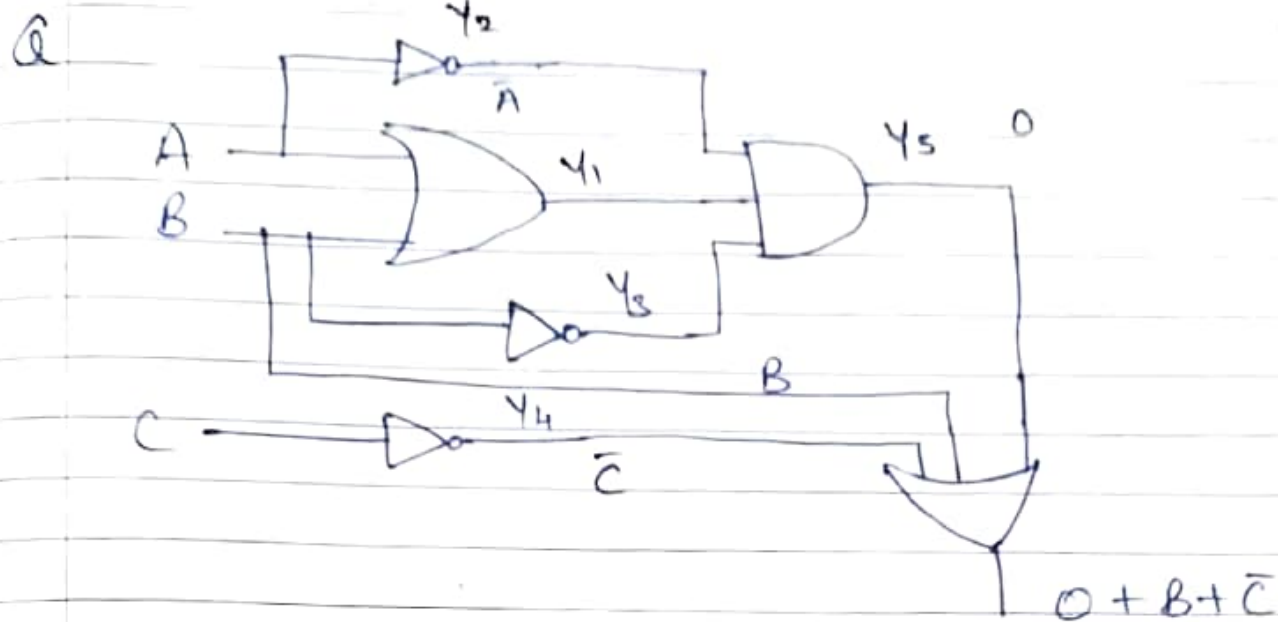

Q


i/p		O/p		
A	B	$Y_1$	$Y_2$	$Y_3$
0	0	0	1	1
0	1	0	0	0
1	0	0	0	0
1	1	1	1	1

$$Y_1 = A \cdot B$$

$$Y_2 = \overline{A \oplus B}$$

$$Y_3 = (A \cdot B) + (\overline{A \oplus B})$$

$$= (A \cdot B) + A \text{ Ex-NOR } B$$

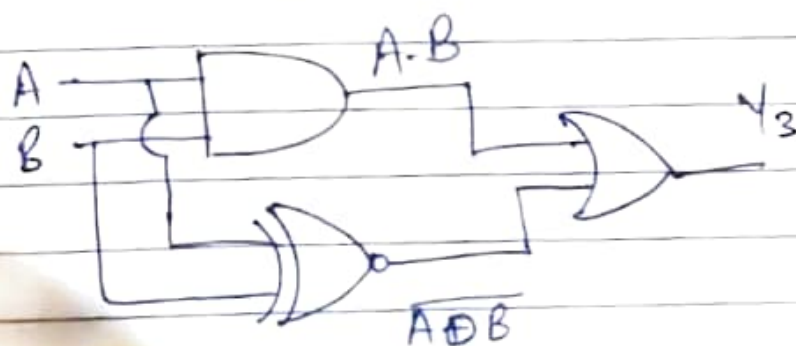

\* SOP = Sum of Products

min terms  $\leftarrow$   $Y = \overset{m_0}{ABC} + \overset{m_1}{AC\bar{B}} + \overset{m_2}{\bar{A}CB}$

$\leftarrow m_0 + m_1 + m_2$  Standard SOP form

SOP form  $\sum m_i$

(For ending)

$AB + B + BC + ABC$

Non Standard SOP form.

\* POS = Product of Sums.

Max terms

$\leftarrow$   $Y = \overset{M_0}{(A+B)} \cdot \overset{M_1}{(B+C)} \cdot \overset{M_2}{(A+C)}$

$Y = \prod M$

$\leftarrow$  Standard POS form.

(For oring)

$A \cdot (A+B) \cdot (A+B+C)$

Non Standard POS form.

A	B	Y
0	0	1
0	1	0
1	0	1
1	1	0

K-Map

Q

A	B	Y
0	0	1
0	1	0
1	0	1
1	1	0

$$\rightarrow \overset{m_0}{A \cdot \bar{B}} + \overset{m_1}{A \cdot B} \quad (\text{using SOP})$$

$$Y = \bar{B} \cdot (A + \bar{A})$$

$$A \cdot \bar{B}$$

Using POS

A	B	Y
0	0	1
0	1	0
1	0	1
1	1	0

$$(A + \bar{B}) \cdot (\bar{A} + \bar{B})$$

$$= A \cdot \bar{A} + A \cdot \bar{B} + \bar{B} \cdot \bar{A} + \bar{B} \cdot \bar{B}$$

$$= 0 + \bar{B}(\bar{A} + A + 1)$$

$$= \bar{B}(1)$$

$$Y = \underline{\underline{\bar{B}}}$$

Q

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Solve By SOP and POS Method.

By SOP

$$\bar{A} \cdot \bar{B} \cdot C + \bar{A} \cdot B \cdot C + A \cdot \bar{B} \cdot \bar{C} + A \cdot \bar{B} \cdot C + A \cdot B \cdot C$$

$$Y = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + ABC$$

$$Y = \bar{A}C(\bar{B}+B) + A\bar{B}(\bar{C}+C) + ABC$$

$$Y = \bar{A}C + A\bar{B} + ABC$$

$$Y = A\bar{B} + \bar{A}C + ABC$$

$$Y = \bar{A}C(B+\bar{B}) + A\bar{B}\bar{C} + AC(\bar{B}+B)$$

$$Y = \bar{A}C + A\bar{B}\bar{C} + AC$$

$$Y = C(\bar{A}+A) + A\bar{B}\bar{C}$$

$$Y = C + A\bar{B}\bar{C}$$

$$Y = (C + \bar{C}) \cdot (C + A\bar{B})$$

$$Y = C + A\bar{B}$$

Using POS

$$(A+B+C) \cdot (A+\bar{B}+C) \cdot (\bar{A}+\bar{B}+\bar{C})$$

$$Y = (A \cdot A + A \cdot \bar{B} + A \cdot C + B \cdot \bar{B} + B \cdot A + B \cdot C + C \cdot A + C \cdot \bar{B} + C \cdot C) \cdot (\bar{A} + \bar{B} + \bar{C})$$

$$Y = (A + A\bar{B} + A \cdot C + 0 + B \cdot A + B \cdot C + C \cdot A + C \cdot \bar{B} + C) \cdot (\bar{A} + \bar{B} + \bar{C})$$

Q

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

SOP

$$A\bar{B} + B\bar{A}$$

POS

~~(A+B)~~


$$(A+B) \cdot (\bar{A} + \bar{B})$$

$$= A\bar{B} + B\bar{A}$$



\* K Map = Karnaugh Map.

A \ B	0	1
0	✓	✓
1	✓	✓

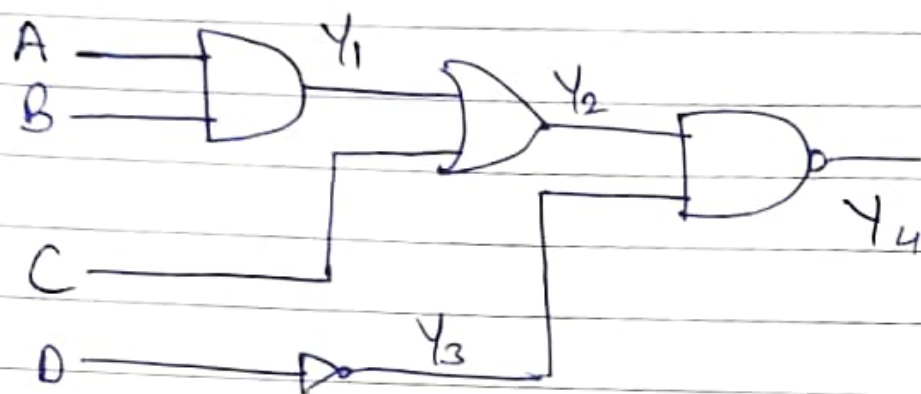

A	B	Y <sub>1</sub>
0	0	0
0	1	0
1	0	0
1	1	1

A

B

SOP

$AB + 0$

$$Y = AB$$

A \ B		0	1
0	0	0	0
1	1	0	1

AB

\* POS Product of Sum

A	B	Y
0	0	0 ✓
0	1	0 ✓
1	0	0 ✓
1	1	1

$$(A+B) \cdot (A+\bar{B}) \cdot (\bar{A}+B)$$

$$= (A+B) \cdot (\cancel{A\bar{A}} + \bar{B}\bar{A} + \cancel{\bar{B}B} + AB)$$

$$= (A+B) \cdot (\bar{B}\bar{A} + AB)$$

$$= A\bar{A}B + A\bar{B}\bar{A} + \cancel{B\bar{B}A} + BAB$$

$$= AB + AB$$

$$= AB$$

A \ B	0	1
0	0	0
1	0	1



A	B	C	$Y_2$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

SOP

A \ BC		$\bar{B}\bar{C}$ 00	$\bar{B}C$ 01	$BC$ 11	$B\bar{C}$ 10
$\bar{A}$	0	0	1	1	0
A	1	0	1	1	1

$$\bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}C + ABC + AB\bar{C}$$

$$= \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}C + ABC + AB\bar{C}$$

$$= \bar{B}C(\bar{A} + A) + BC(\bar{A} + A) + AB\bar{C}$$

$$A + \bar{A}B = A + B$$

$$= \bar{B}C + BC + AB\bar{C}$$

$$= C(\bar{B} + B) + AB\bar{C}$$

$$= C + AB\bar{C}$$

$$= C + \bar{C}AB$$

$$= (C + \bar{C}) \cdot (C + AB)$$

$$= C + AB \Rightarrow AB + C$$

POS

		$(B+C)$	$(B+\bar{C})$	$(\bar{B}+C)$	$(\bar{B}+\bar{C})$
		00	01	11	10
A	0	0	1	1	0
$\bar{A}$	1	0	1	1	1

$$(A+B+C) \cdot (\bar{A}+B+C) \cdot (\bar{A}+\bar{B}+C)$$

$$(A+B+C) \cdot (\bar{A}+B+C) \cdot (A+\bar{B}+C)$$

$$[B+C](A+\bar{B}+C)$$

$$AB + AC + \overset{0}{\cancel{BB}} + \bar{B}C + C\bar{B} + C \cdot C$$

$$= AB + C[A + \bar{B} + B + 1]$$

$$= AB + C$$

23/3/23

			Min. terms SOP	Max. terms POS
A	B	C		
0	0	0	$\bar{A}\bar{B}\bar{C}$ $m_0$	$A+B+C$
0	0	1	$\bar{A}\bar{B}C$ $m_1$	$A+B+\bar{C}$
0	1	0	$\bar{A}B\bar{C}$ $m_2$	$A+\bar{B}+C$
0	1	1	$\bar{A}BC$ $m_3$	$A+\bar{B}+\bar{C}$
1	0	0	$A\bar{B}\bar{C}$ $m_4$	$\bar{A}+B+C$
1	0	1	$A\bar{B}C$ $m_5$	$\bar{A}+B+\bar{C}$
1	1	0	$AB\bar{C}$ $m_6$	$\bar{A}+\bar{B}+C$
1	1	1	$ABC$ $m_7$	$\bar{A}+\bar{B}+\bar{C}$

		BC			
		$B+C$ $\bar{B}\bar{C}$ 00	$B+\bar{C}$ $\bar{B}C$ 01	$\bar{B}+C$ $BC$ 11	$\bar{B}+\bar{C}$ $\bar{B}\bar{C}$ 10
A	$\bar{A}$	0 $m_0$	1 $m_1$	1 $m_3$	0 $m_2$
$\bar{A}$	A	0 $m_4$	1 $m_5$	1 $m_7$	1 $m_6$

Pair → reduces by 1  
 Quad → reduces by 2  
 Octa → reduces the no. of variables by 3 in the expression

Pair → reduces by 1  
 Quad → reduces by 2  
 Octa → reduces the no. of variables by 3 in the expression



Q			$\bar{B}\bar{C}$	$B+\bar{C}$	$\bar{B}+\bar{C}$	$B\bar{C}$
POS	SOP	A \ BC	00	01	11	10
A	$\bar{A}$	0	1	0	0	1
$\bar{A}$	A	1	1	0	0	1

Q			$\bar{C}+\bar{D}$	$C+\bar{D}$	$\bar{C}+\bar{D}$	$\bar{C}+\bar{D}$
POS	SOP	AB \ CD	00	01	11	10
$A+\bar{B}$	$\bar{A}\bar{B}$	00	1	0	0	1
$A+\bar{B}$	$\bar{A}\bar{B}$	01	0	1	1	0
$A+\bar{B}$	$\bar{A}\bar{B}$	11	0	1	1	0
$A+\bar{B}$	$\bar{A}\bar{B}$	10	1	0	0	1

$$BD + \bar{B}\bar{D}$$

$$B \oplus D = B \cdot 0 \cdot D$$

$$(B + \bar{D}) \cdot (D + \bar{B})$$